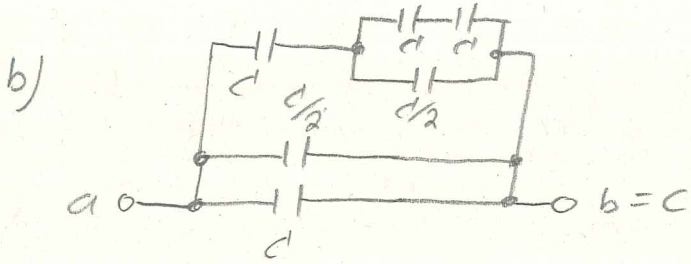


① a) $C_{bc} = 0$



$$C_{ab} = 2d$$

c)

$$C_{ac} = C_{ab} = 2d$$

d)


$$R_i = \frac{R_1 R_3 + R_1 R_4 + R_3 R_4}{R_1 + R_3}$$

e)


$$\frac{I_k}{I_{on}} = \frac{R_1 \parallel R_3 \parallel R_4}{R_4} \Rightarrow I_k = I_{on} \cdot \frac{R_1 R_3}{R_1 R_3 + R_1 R_4 + R_3 R_4}$$

f)

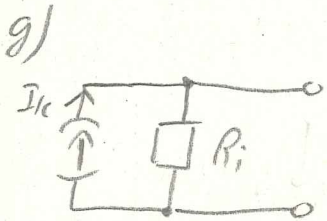
$$U_L = I_k \cdot R_i = I_{on} \cdot \frac{R_1 R_3}{R_1 + R_3}$$



2. a)

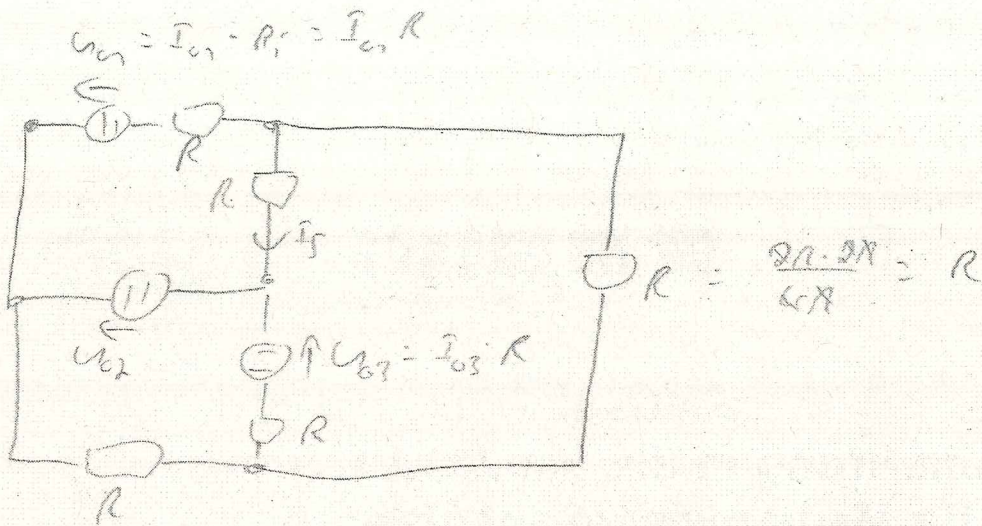

b)

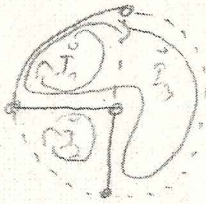

$$c) m = 2 - (k - 1) = 3$$

$$\begin{aligned} U_{01} &= 4V \\ U_{02} &= 2V \\ U_{03} &= 1V \end{aligned}$$

$$d) \begin{pmatrix} 2R & 0 & R \\ 0 & 2R & -R \\ R & -R & 3R \end{pmatrix} \begin{pmatrix} \vec{I}_1 \\ \vec{I}_2 \\ \vec{I}_3 \end{pmatrix} = \begin{pmatrix} U_{01} - U_{02} \\ U_{02} + U_{03} \\ U_{01} - U_{02} - U_{03} \end{pmatrix}$$

$$e) \vec{I}_5 = \vec{I}_1$$

$$\underline{D} = \det \begin{pmatrix} 2R & 0 & R \\ 0 & 2R & -R \\ R & -R & 3R \end{pmatrix} = 12R^3 + 0 + 0 - (2R^3 + 2R^3 + 0) = 8R^3 = 1000 R^3$$

$$\begin{aligned} D_1 &= \det \begin{pmatrix} U_{01} - U_{02} & 0 & R \\ U_{02} + U_{03} & 2R & -R \\ U_{01} - U_{02} - U_{03} & -R & 3R \end{pmatrix} = 2V \cdot 100\Omega \cdot 150\Omega + 0 + 50\Omega \cdot 3V \cdot (-50\Omega) \\ &\quad - (1V \cdot 100\Omega \cdot 50\Omega + (-50\Omega) \cdot (-50\Omega) \cdot 2V + 0) \\ &= 30kV\Omega^2 + (-7,5kV\Omega^2) - 5k\Omega^2 - 5k\Omega^2 \\ &= 12,5kV\Omega^2 = 12,5kA\Omega^3 \end{aligned}$$

$$\underline{\underline{\vec{I}_1 = \vec{I}_5 = \frac{D_1}{D} = \frac{12,5kA\Omega^3}{1000k\Omega^3} = 12,5mA}}$$

3. a) $H(s\omega) = \frac{y_2(s\omega)}{y_1(s\omega)} = \frac{R/c}{R + (R/c)} = \frac{1}{2 + s\omega cR}$

b) $|H(s\omega)| = \frac{1}{\sqrt{4 + \omega^2 c^2 R^2}} ; \varphi(\omega) = -\arctan\left(\frac{\omega cR}{2}\right)$


c) $\underline{\omega=0}: H(s\omega=0) = \frac{1}{2} \quad \varphi(\omega=0) = 0$

$\underline{\omega \rightarrow \infty}: H(s\omega \rightarrow \infty) = 0 \quad \varphi(\omega \rightarrow \infty) = -\frac{\pi}{2}$

$\underline{\omega_g}: H(s\omega_g) = \frac{1}{\sqrt{2}} \cdot H_{max} = \frac{1}{\sqrt{2}} \cdot \frac{1}{2}$


$\Rightarrow \frac{1}{\sqrt{2}} \cdot \frac{1}{2} = \frac{1}{\sqrt{4 + (\omega_g cR)^2}} \Rightarrow \underline{\underline{\omega_g = \frac{2}{cR}}}$

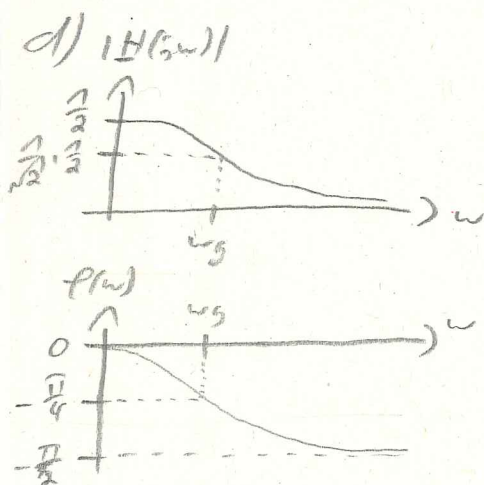$\underline{\underline{\varphi(\omega_g) = -\frac{\pi}{4}}}$



e) Tiefpass


4) a) $u_c(t=0+) = u_c(t=0-) = 2U_0$

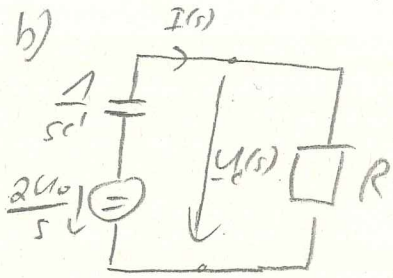

c) $\frac{u_c(s)}{2 \frac{U_0}{s}} = \frac{R}{R + \frac{1}{sC}} \Rightarrow u_c(s) = 2U_0 \cdot \frac{1}{s + \frac{1}{RC}}$

d) $u_c(t) = 2U_0 \cdot e^{-\frac{1}{RC}t}, t \geq 0$

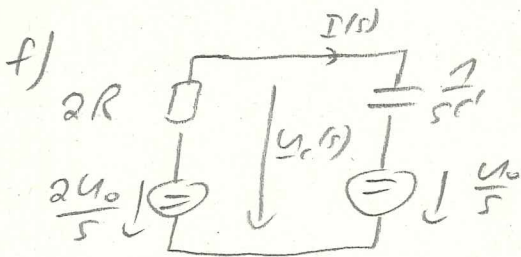e) $\underline{u_c(t=T)} = 2U_0 \cdot e^{-\frac{1}{50k\Omega \cdot 40\mu F} \cdot 1,38625} = 2U_0 \cdot 0,5 = \underline{U_0}$



g) $I(s) = \frac{\frac{2U_0}{s} - \frac{U_0}{s}}{2R + \frac{1}{sC}} = \frac{U_0}{s} \cdot \frac{sC}{2sRC + 1}$

$\underline{u_c(s)} = I \cdot \frac{1}{sC} \cdot e^{-sT} + \frac{U_0}{s} = \frac{U_0}{s} \cdot \frac{\frac{1}{2RC}}{s + \frac{1}{2RC}} \cdot e^{-sT} + \frac{U_0}{s}$

h) $u_c(t) = U_0 \cdot (1 - e^{-\frac{1}{2RC}(t-T)}) + U_0, t \geq T$

