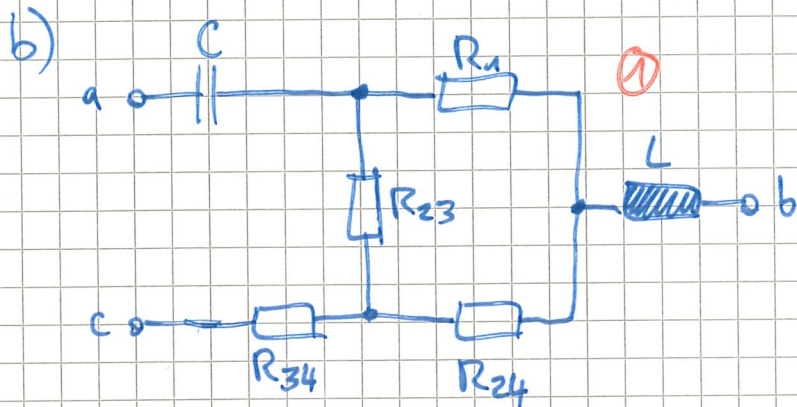


$$\begin{aligned}
 1a) \quad Z_{ab} &= \frac{1}{j\omega C} + R_1 \parallel R_2 \parallel (R_3 + R_4) + j\omega L \quad (1) \\
 &= 0,5 R \parallel (b_1 + 1) R + j(\omega L - \frac{1}{\omega C}) \\
 &= \frac{\frac{b_1 + 1}{2}}{(b_1 + 1,5)} R + j(\omega L - \frac{1}{\omega C}) \quad (1)
 \end{aligned}$$



$$\begin{aligned}
 R_{23} &= \frac{R_2 \cdot R_3}{R_2 + R_3 + R_4} = \frac{1}{b_1 + 2} R \\
 R_{34} &= \frac{R_3 \cdot R_4}{R_2 + R_3 + R_4} = \frac{b_1}{b_1 + 2} R \\
 R_{24} &= \frac{R_2 \cdot R_4}{R_2 + R_3 + R_4} = \frac{b_1}{b_1 + 2} R \quad (1)
 \end{aligned}$$

$$\begin{aligned}
 Z_{ac} &= \frac{1}{j\omega C} + R_{23} \parallel (R_1 + R_{24}) + R_{34} \quad (1) \\
 &= \frac{R_{23} (R_1 + R_{24})}{R_{23} + R_1 + R_{24}} + R_{34} - j \frac{1}{\omega C} \\
 &= \frac{\frac{1}{b_1 + 2} (1 + \frac{b_1}{b_1 + 2})}{\frac{b_1 + 1}{b_1 + 2} + 1} R + \frac{b_1}{b_1 + 2} R - j \frac{1}{\omega C} \\
 &= \left(\frac{2b_1 + 2}{(b_1 + 2)(2b_1 + 3)} + \frac{b_1}{b_1 + 2} \right) R - j \frac{1}{\omega C} \quad (1)
 \end{aligned}$$

$$\begin{aligned}
 c) \quad Z_{bc} &= j\omega L + R_{24} \parallel (R_1 + R_{23}) + R_{34} \quad (1) \\
 &= \left(\frac{2b_1 + 2}{(b_1 + 2)(2b_1 + 3)} + \frac{b_1}{b_1 + 2} \right) R + j\omega L \quad (1)
 \end{aligned}$$


e) $\omega L = \frac{1}{\omega C} \Rightarrow L = \frac{1}{\omega^2 C} = \mu \frac{w^2 h}{2\pi} \ln\left(\frac{r_2}{r_1}\right) \quad (1)$

$$\Rightarrow w = \sqrt{\frac{1}{\omega^2 C} \cdot \frac{2\pi}{\mu h \ln\left(\frac{r_2}{r_1}\right)}} = 100,13$$


$$l = w \cdot \frac{1}{\lambda} = 100,13 \cdot \frac{1}{10^3 \text{ cm}} = 10,02 \text{ cm} \quad (1)$$

$$\begin{aligned}
 d) \quad L &= \mu \frac{w^2 h}{2\pi} \ln\left(\frac{r_2}{r_1}\right) = \mu \frac{(l \cdot \frac{w}{\lambda})^2 h}{2\pi} \ln\left(\frac{r_2}{r_1}\right) \\
 &= 1 \mu\text{H} \quad (1)
 \end{aligned}$$

2a)

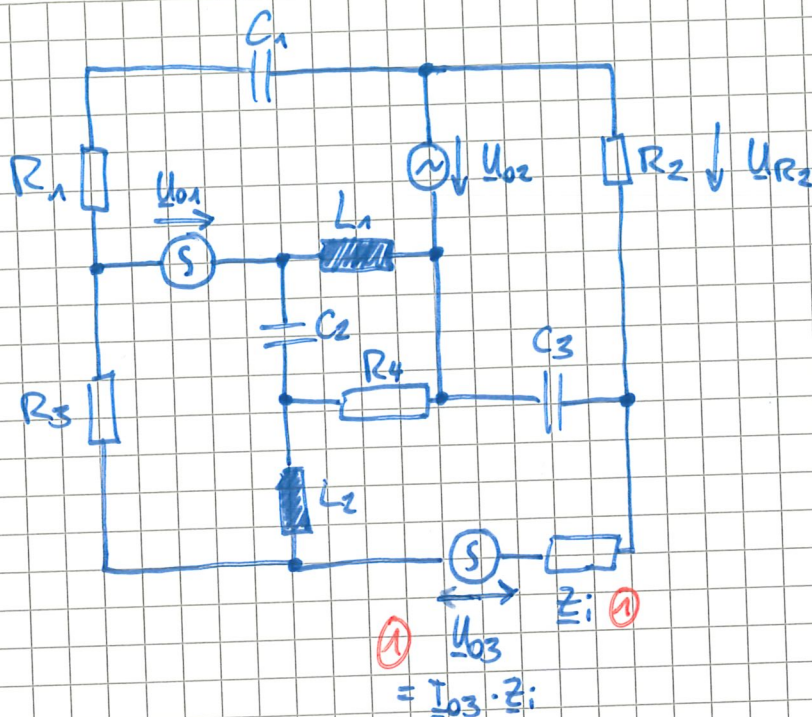

b)

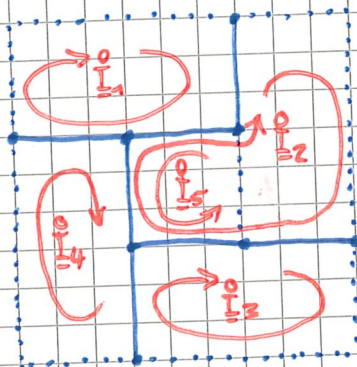

... Graph ①

— Baum ①

c)

$$m = z - k + 1 = 12 - 8 + 1 = 5 \quad ①$$

Maschendefinitionen ①

d)

$$\begin{pmatrix} R_1 + j(\omega L_1 - \frac{1}{\omega C_1}) & 0 & 0 & 0 & 0 \\ -j\omega L_1 & R_2 + R_4 + j(\omega L_1 - \frac{1}{\omega C_1}) & j\frac{1}{\omega C_3} + R_4 & 0 & 0 \\ 0 & j\frac{1}{\omega C_3} & R_4 + j(\omega L_2 - \frac{1}{\omega C_3}) + Z_i & 0 & 0 \\ 0 & 0 & -j\omega L_2 & R_3 + j(\omega L_2 - \frac{1}{\omega C_2}) & -j\frac{1}{\omega C_2} \\ j\omega L_1 & 0 & 0 & -j\frac{1}{\omega C_2} & R_4 + j(\omega L_1 - \frac{1}{\omega C_2}) \end{pmatrix} \begin{pmatrix} U_{o1} - U_{o2} \\ U_{o2} \\ I_{o3} \cdot Z_i \\ -U_{o1} \\ 0 \end{pmatrix}$$

Diagonale ②
Abstandelemente ②
Spannungen ①

e) $I_{R3} = I_4 \quad ①$

$U_{R2} = R_2 I_2 \quad ①$

$$f) R \dot{I}_1 + j10R \dot{I}_2 = -U_{01}$$

$$j10R \dot{I}_1 + j10R \dot{I}_3 = 0 \Rightarrow \dot{I}_1 = -\dot{I}_3$$

$$j10R \dot{I}_2 + (b_2 + j10)R \dot{I}_3 = I_{02}R$$

$$-jR \dot{I}_3 + j10R \dot{I}_2 = -U_{01} \Rightarrow \dot{I}_2 = \frac{jR \dot{I}_3 - U_{01}}{j10R}$$

$$\cancel{j10R} \frac{jR \dot{I}_3 - U_{01}}{\cancel{j10R}} + (b_2 + j10)R \dot{I}_3 = I_{02}R$$

$$\dot{I}_3 = \frac{I_{02}R + U_{01}}{(b_2 + j11)R} = \frac{1}{b_2 + j11} \cdot 36 \text{ mA} \quad \textcircled{1}$$

$$\dot{I}_1 = -\frac{1}{b_2 + j11} \cdot 36 \text{ mA} \quad \textcircled{1}$$

$$\dot{I}_2 = \frac{\dot{I}_3}{10} - \frac{U_{01}}{j10R} = \frac{1}{b_2 + j11} \cdot 3,6 \text{ mA} + j2,4 \text{ mA}$$

$$= \left(\frac{3}{b_2 + j11} + j2 \right) \cdot 1,2 \text{ mA} \quad \textcircled{1}$$

$$3a) \underline{H}(j\omega) = \frac{U_2}{U_1} = \frac{j\omega L}{j(\omega L - \frac{1}{\omega C})} = \frac{\omega L}{\omega L - \frac{1}{\omega C}} \quad (1)$$

$$b) |\underline{H}(j\omega)| = \frac{\omega L}{\omega L - \frac{1}{\omega C}} = \frac{\omega^2 L}{\omega^2 L - \frac{1}{C}} \quad (1)$$

$$\varphi(\omega) = 0 \quad (1)$$

$$c) \omega = 0:$$

$$|\underline{H}(j\omega=0)| = 0 \quad (1)$$


$$\varphi(\omega=0) = 0 \quad (1)$$

$$\omega \rightarrow \infty:$$

$$|\underline{H}(j\omega \rightarrow \infty)| = 1 \quad (1)$$

$$\varphi(\omega \rightarrow \infty) = 0 \quad (1)$$

Übertragungsverhalten: Hochpass (1)

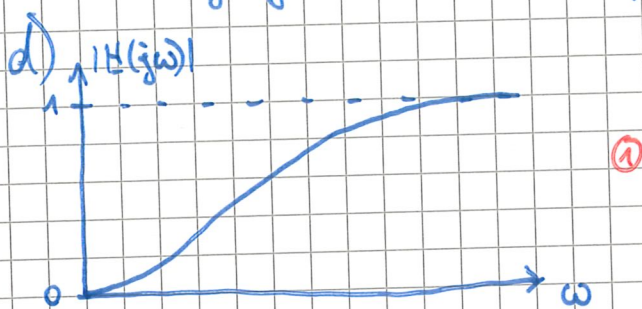

$$e) \underline{Z}_i = b_1 R + j\omega L \parallel \frac{1}{j\omega C} = b_1 R + \frac{\frac{L}{C}}{j(\omega L - \frac{1}{\omega C})} = b_1 R - j \frac{L/C}{\omega L - \frac{1}{\omega C}} \quad (1)$$

$$f) \underline{U}_L = \underline{U}_{in} \cdot \underline{H}(j\omega) = \underline{U}_{in} \cdot \frac{\omega L}{\omega L - \frac{1}{\omega C}} \quad (1)$$


$$\underline{I}_k = \frac{\underline{U}_L}{\underline{Z}_i} = \frac{\underline{U}_{in} \frac{\omega L}{\omega L - \frac{1}{\omega C}}}{b_1 R - j \frac{L/C}{(\omega L - \frac{1}{\omega C})}} = \frac{\underline{U}_{in} \omega L}{b_1 R (\omega L - \frac{1}{\omega C}) - j \frac{L}{C}} \quad (1)$$

$$g) \underline{U}_{last} = \underline{U}_L \cdot \frac{\underline{Z}_{last}}{\underline{Z}_{last} + \underline{Z}_i} = \underline{U}_L \cdot \frac{\underline{Z}_i^*}{\underline{Z}_i^* + \underline{Z}_i} \quad (1)$$

$$= \underline{U}_{in} \frac{\omega L}{\omega L - \frac{1}{\omega C}} \cdot \frac{b_1 R + j \frac{L}{C}}{2b_1 R}$$

$$= \frac{1}{2} \underline{U}_{in} \frac{\omega L}{\omega L - \frac{1}{\omega C}} \cdot \left(1 + j \frac{L}{b_1 R (\omega L - \frac{1}{\omega C})} \right) \quad (1)$$

4a) $u_1(0+) = U_{01}$ ①

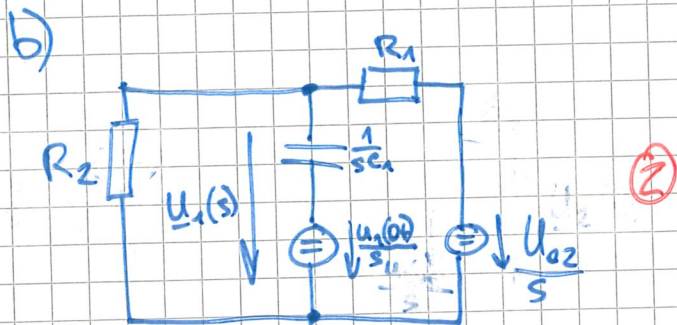

c) $\underline{U}_1(s) = \underline{U}_{u1}(s) + \underline{U}_{u2}(s)$ ①

• $\underline{U}_{u1}(s)$ bei $\frac{U_{02}}{s} = 0$:

$$\frac{\underline{U}_{u1}(s)}{\frac{U_{01}(0+)}{s}} = \frac{R_1 \parallel R_2}{\frac{1}{sC_1} + R_1 \parallel R_2} = \frac{\frac{R_1 R_2}{R_1 + R_2}}{\frac{1}{sC_1} + \frac{R_1 R_2}{R_1 + R_2}} = \frac{1}{\frac{1}{sC_1} \cdot \frac{R_1 + R_2}{R_1 R_2} + 1}$$

$$= \frac{s}{\frac{R_1 + R_2}{C_1 R_1 R_2} + s}$$

$$\underline{U}_{u1}(s) = \frac{U_{01}(0+)}{s} \cdot \frac{s}{s + \frac{R_1 + R_2}{C_1 R_1 R_2}} = U_{01}(0+) \frac{1}{s + c} \text{ mit } c = \frac{R_1 + R_2}{C_1 R_1 R_2} \quad ①$$

• $\underline{U}_{u2}(s)$ bei $\frac{U_{01}}{s} = 0$:

$$\frac{\underline{U}_{u2}(s)}{\frac{U_{02}}{s}} = \frac{R_2 \parallel \frac{1}{sC_1}}{R_1 + R_2 \parallel \frac{1}{sC_1}} = \frac{\frac{R_2}{sC_1}}{R_1 + \frac{R_2}{sC_1}} = \frac{\frac{R_2}{sC_1}}{R_1 + \frac{R_2}{sC_1}}$$

$$= \frac{R_2}{R_2 + R_1(sC_1 R_2 + 1)} = \frac{R_2}{s C_1 R_1 R_2 + R_1 + R_2}$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{s C_1 R_1 R_2 + R_1 + R_2} = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{R_1 + R_2}{C_1 R_1 R_2}}{s + \frac{R_1 + R_2}{C_1 R_1 R_2}}$$

$$\underline{U}_{u2}(s) = U_{02} \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{c}{s(s + c)} \text{ mit } c = \frac{R_1 + R_2}{C_1 R_1 R_2} \quad ①$$

d) $u_1(t) = U_{01} \cdot e^{-\frac{R_1 + R_2}{C_1 R_1 R_2} t} + U_{02} \frac{R_2}{R_1 + R_2} \left(1 - e^{-\frac{R_1 + R_2}{C_1 R_1 R_2} t} \right); t \geq 0$

$$= U_{02} \frac{R_2}{R_1 + R_2} + \left(U_{01} - U_{02} \frac{R_2}{R_1 + R_2} \right) \cdot e^{-\frac{R_1 + R_2}{C_1 R_1 R_2} t}; t \geq 0 \quad ①$$

e) $u_1(t \rightarrow \infty) = U_{02} \frac{R_2}{R_1 + R_2} \quad ①$

f) $u_1(t^*) = U_{02} \frac{R_2}{R_1+R_2} + (U_{01} - U_{02} \frac{R_2}{R_1+R_2}) \cdot e^{-ct^*}$ mit $c = \frac{R_1+R_2}{C_1 R_1 R_2}$

$$\Rightarrow t^* = - \frac{C_1 R_1 R_2}{R_1+R_2} \ln \left(\frac{u_1(t^*) - U_{02} \frac{R_2}{R_1+R_2}}{U_{01} - U_{02} \frac{R_2}{R_1+R_2}} \right) \quad (1)$$

$$= b_2 \cdot 0,3 \text{ s} \quad (1)$$

